

# Lab 15 finding

**Sepideh Mohammadi**  
ECEN 5730  
PCB DESIGN

Data collected from a Hex inverter high speed digital circuit



# Overview:


## Good and bad switching noise

- Objective:  
To investigate how PCB layout (good vs. bad return path and decoupling) affects switching noise, rise time and fall time, and rail stability in high-speed digital circuits.
- This experiment demonstrates the importance of good layout practices, such as solid return planes and close decoupling, in minimizing noise and improving switching speed.
 
# Overview of circuit:

---


- Quality\_Metric: Compare the rise/fall times as well as the rail collapse of each of the three blocks
  - Good layout= Close decoupling, solid return plane
  - GOOD but Cap far = Far decoupling, solid return plane
  - Bad Bad = Far decoupling, no return plane


 
# Key finding:

Rise/fall times were measured for both good and bad PCB layouts using the 555-timer trigger.

**Key message: Good layout → fast, clean transitions.  
Bad layout → slower edges and larger rail noise from poor return paths and decoupling.**



Layout	Rise Time (ns)	Vp-p Rail Collapse (mV)	Relative to Good Layout
Good Layout	2.25 ns	274	Reference (1x)
Good but Cap Far	3.77 ns	1031	1.7x slower, 5x more noise
Bad Layout	4.86 ns	709	2.2x slower, 2.6x more noise

# Summary



In this experiment, we measured how PCB layout quality affects switching speed and rail stability.

Despite identical circuits, layout differences caused significant variation in performance.

- The bad layout showed 2.2× slower rise time and nearly 2× higher rail noise compared to the good layout.
- The good but cap far layout also degraded performance, showing ~1.7× slower edges and larger rail collapse, confirming the importance of short decoupling paths.
- The good layout maintained the fastest transitions and most stable voltage rails due to proper decoupling and short return paths.
- All future designs should prioritize tight decoupling placement and continuous ground planes, as these design practices dramatically improve signal integrity and reduce switching noise.

# Full Results:

Layout	Rise Time (ns)	Voltage Rail Collapse (Pk-Pk mV)	Scope Ref.	Fall Time (ns)	Voltage Rail Collapse (Pk-Pk mV)	Scope Ref.
Good Layout	2.25	274	Scope 0	1.89	181	Scope 1
Bad Layout	4.86	1031	Scope 2	3.92	2763	Scope 3
Good but Cap Far	3.78	709	Scope 4	2.47	829	Scope 5

  

555 clock

Bad layout

Good layout

Good but cap far

555 clock

Bad layout

Good layout

Good but cap far

555 clock

Bad layout

Good layout

Good but cap far

